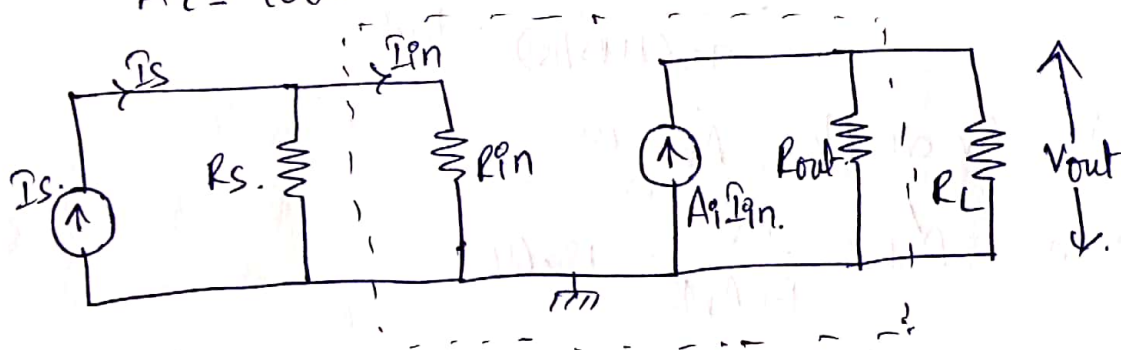


# Tutorial

4/1/19.

(1) A current Amplifier has an i/p resistance of  $10\Omega$ , and an o/p resistance of  $10k\Omega$  and a current gain of 1000. It is fed by a current source having a source resistance of  $10k\Omega$  and its o/p is connected to a  $10\Omega$  load resistance. Find the voltage gain and power gain.

sol  $R_s = 10k\Omega$ ,  $R_{in} = 10\Omega$ ,  $R_{out} = 10k\Omega$ ,  $R_L = 10\Omega$ .  
 $A_i = 1000$ .



i/p voltage  $V_{in} = I_{in} R_{in} = 10 \cdot I_{in} \text{ V.}$

o/p voltage  $V_{out} = A_i I_{in} (R_{out} \parallel R_L) = A_i I_{in} \cdot \frac{R_{out} \times R_L}{R_{out} + R_L}$   
 $= 1000 I_{in} \cdot \frac{10k \times 10}{10k + 10} = 9990 I_{in} \text{ V.}$

$A_v = \frac{V_{out}}{V_{in}} = \frac{9990 I_{in}}{10 I_{in}} = 999.$

the current gain  $A_I = \frac{I_L}{I_s} = \frac{\frac{V_{out}}{R_L}}{I_{in} \left( \frac{R_s + R_{in}}{R_s} \right)} = \frac{9990 I_{in}}{10 \times \left( \frac{10k + 10}{10k} \right) \cdot I_{in}}$

$A_I = 998.$

power gain  $A_p = A_v \cdot A_I = 997 \times 10^3.$

(2) Calculate the gain of a negative feedback amplifier with an internal gain  $A_v = 75$  and feedback fraction  $m_v = 1/15$ . What will be the gain if  $A_v$  doubles?

Sol

open loop voltage gain  $A_v = 75$ .

feedback fraction  $\beta = \frac{1}{75}$

negative feedback voltage gain  $A_f = \frac{A_v}{1 + A_v \beta}$

$$= \frac{1}{75(1 + 75/15)} = 12.5$$

if  $A_v$  doubles  $A_v' = 150$ .

then  $A_f' = \frac{A_v'}{1 + A_v' \beta} = 13.64$

(3) An amplifier has a voltage gain of 40. The amplifier is now modified to provide a 10% negative feedback in series with the i/p. Find (i) voltage gain with feedback (ii) amount of feedback in dB, (iii) loop gain.

Sol

$$A = 40$$

$$\text{feedback } 10\% = 0.1$$

$$A_f = \frac{A}{1 + \beta A} = 8$$

$$\text{Amount of feedback} = \frac{1}{1 + \beta A}$$

$$\text{in dB} = 20 \log \left( \frac{1}{1 + \beta A} \right) = -13.98$$

$$\text{loop gain} = \beta A = 40 \times 0.1 = 4$$

(3)

Q The voltage gain of an amplifier without feedback is 2500.  
If 40dB of negative feedback is added. Find

(i)  $A_f$ .

(ii) for obtaining the same o/p, how much must be the i/p increased.

Sol.

$$A = 2500.$$

Desensitivity of transfer gain  $\cdot (1 + A\beta)$

$$= \text{antilog} \left( \frac{40}{20} \right) = 100.$$

$$A_f = \frac{2500}{100} = 25.$$

The i/p for same o/p will become  $A/A_f$  times the i/p ~~was~~ without feedback i.e.  $\frac{2500}{25} = 100$  times the i/p without feedback.