

Tutorial -

1. A feedback amplifier has a voltage gain of 500 without feedback. Determine the voltage gain with feedback if feedback ratio = 0.1

$$A_f = \frac{A}{1 + A\beta} = \underline{\underline{9.8}}$$

2. In a negative feedback amplifier $A = 100$, $\beta = 0.02$ & i/p signal voltage is 40mV. Determine (i) voltage gain with feedback (ii) feedback factor (iii) feedback voltage & (iv) o/p voltage.

Sol. Given $A = 100$ $\beta = 0.02$
 $V_s = 40\text{mV}$

$$\Rightarrow \text{(i)} \Rightarrow A_f = \frac{A}{1 + A\beta} = \underline{\underline{33.33}}$$

$$\text{(ii)} \Rightarrow \frac{A\beta}{\beta} = \frac{100 \times 0.02}{0.02} = \underline{\underline{2}}$$

$$\text{(iii)} \Rightarrow V_f = \beta V_o \Rightarrow 26.66\text{mV}$$

$$\text{(iv)} \Rightarrow V_o = A_f \cdot V_{in} = 33.33 \times 40\text{mV} = 1.33\text{V}$$

3. An Amplifier has gain of 60 & distortion 10% without feedback. Determine (1) closed loop gain, (2) Distortion when a negative feedback is applied to feedback factor being 6

Sol.

$$A = 60$$

$$D = 10\% = 0.1$$

$$A_f = \frac{A}{1 + A\beta} = 8.57$$

$$D_f = \frac{D}{1 + A\beta} = 1.42\%$$

4) An Amplifier has midband gain of 200 without feedback. The 3 dB frequency width of it is 200k. The amplifier is to be used as a video amplifier that requires 5MHz bandwidth. what gain can be obtained & what feedback must be used? what bandwidth could be obtained if the feedback were 100%.

Sol $A_v = 200$

$BW_f = 5\text{MHz}$

$BW = 200\text{k}$

$$BW_f = (1 + A\beta) BW$$

$$\beta = \left(\frac{BW_f}{BW} - 1 \right) \frac{1}{A} = 0.12$$

$$A_f = \frac{A}{1 + A\beta} = 8$$

if $\beta = 100\% = 1$

$$BW_f = (1 + A\beta) BW = 40.2\text{MHz}$$