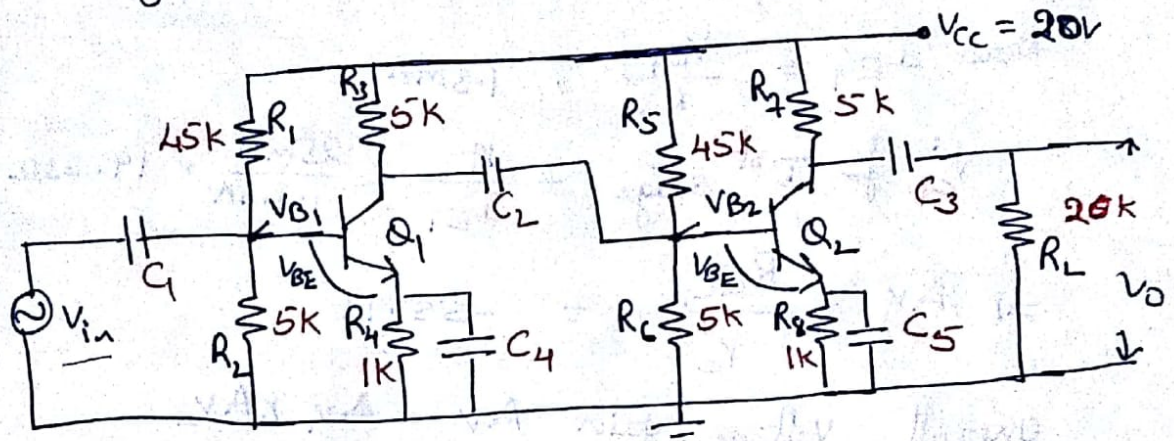


Unit - 2 - Multistage Amplifiers

①

1. Compute the overall voltage gain for the 2-stage R-C Coupled amplifier shown in fig. Express the gain in dBs. by considering $V_{BE} = 0.7V$ & $\beta_1 = \beta_2 = 100$.



Sol 1-

(i) V_{B2} voltage across B of Q_2

$$V_{B2} = \frac{V_{CC} \cdot R_6}{R_5 + R_6} = 2V$$

$$\Rightarrow V_{E2} = V_{B2} - V_{BE} = 2 - 0.7 = 1.3V$$

$$\text{Now } I_{E2} \text{ across } R_8 \Rightarrow I_{E2} = \frac{V_{E2}}{R_8} = 1.3mA$$

$$\Rightarrow \text{the } r'_{e2} = \frac{V_T}{I_{E2}} = \frac{25mV}{1.3mA} = 19.23\Omega \quad [r'_e \text{ internal forward resistance}]$$

$$\Rightarrow Z_{in(B2)} \text{ for 2nd stage} = \beta r'_{e2} = 1.923k\Omega$$

\Rightarrow i/p impedance for 2nd stage

$$Z_{in2} = R_5 \parallel R_6 \parallel Z_{in(B2)} = 1.347k$$

Effective collector load for 2nd stage

$$R_{ac2} = R_7 \parallel R_L = 4k\Omega$$

$$\text{voltage gain of 2nd stage } A_{V2} = - \frac{R_{ac2}}{r'_{e2}} = -208$$

output collector load for I^{st} stage

$$R_{ac1} = R_3 // z_{in2} = 1.06 k\Omega$$

$$V_{B1} = \frac{V_{CC} R_2}{R_1 + R_2} = 2V$$

$$V_{E1} = V_{B1} - V_{BE} = 1.3V$$

$$\text{Now } I_{E1} = \frac{V_{E1}}{R_4} = 1.3mA$$

$$r'_{e1} \text{ for } I^{st} \text{ stage} = \frac{V_T}{I_{E1}} = \frac{25mV}{1.3mA} = 19.23\Omega$$

$$\Rightarrow A_{V1} = \frac{R_{ac1}}{r'_{e1}} = -55.12$$

$$\text{Overall voltage gain } A_V = A_{V1} \times A_{V2} = 11,465$$

$$\text{gain in dBs} = 81.2dB$$

2. The RC Coupled amplifier has Mid freq gain = 100. The values of lower & upper cutoff freq are $f_1 = 80Hz$ & $f_2 = 80kHz$. Find the freq at which the gain is reduced to 80.

$$\text{Given } (A_V)_m = 100 ; f_1 = 80Hz \quad f_2 = 80kHz$$

$$\text{where } (A_V)_d = \frac{(A_V)_m}{\sqrt{1 + (f_1/f)^2}} = \frac{(A_V)_m^2}{(A_V)_d^2} = 1 + (f_1/f)^2$$

$$\frac{(A_V)_m^2}{(A_V)_d^2} - 1 = (f_1/f)^2$$

$$\Rightarrow f = \frac{f_1 (A_V)_d}{\sqrt{(A_V)_m + (A_V)_d} (A_V)_m - (A_V)_d}$$

$$A_{Vd} = A_{Vh} = 80$$

$$\text{Hence } (A_V)_h = \frac{(A_V)_m}{\sqrt{1 + (f'/f_2)^2}} \Rightarrow f' = f_2 \sqrt{\frac{(A_V)_m + (A_V)_h}{(A_V)_h}}$$

(3) 3 - identical stages in a multistage amplifier have an overall upper 3dB freq of 40KHz & lower 3dB freq of 15KHz . what is the operating bandwidth of each amplifier stage?

no of stages $n = 3$

overall lower 3dB freq $f_1^n = 15\text{KHz}$

overall upper 3dB freq $f_2^n = 40\text{KHz}$

$$\Rightarrow f_1^n = \frac{f_1}{\sqrt{2^{1/n} - 1}} \Rightarrow f_1 = f_1^n \sqrt{2^{1/n} - 1}$$

$$\Rightarrow f_2^n = \frac{f_2}{\sqrt{2^{1/n} - 1}} \Rightarrow f_2 = f_2^n / \sqrt{2^{1/n} - 1}$$