

⇒ SIMPLIFIED CE HYBRID MODEL:

As the h -parameters themselves vary widely for the same type of transistor, it is justified to make approximations and simplify the expressions for A_I , A_V , R_i & R_o .

In addition, a better understanding of the behavior of the transistor circuit can be obtained by using the simplified hybrid model.

Since CE configuration is more useful & general, it is taken for consideration.

The h -parameter equivalent circuit of the transistor in the CE configuration is shown in fig. above called exact model.

→ Here, $1/h_{oe}$ is in parallel with R_L . The parallel combination of two unequal impedances i.e. $1/h_{oe}$ & R_L is \approx to the lower value i.e. R_L $\because 1/h_{oe} \gg R_L$.
Hence if $1/h_{oe} \gg R_L$ then the term h_{oe} may be neglected.

i.e. $h_{oe} R_L \ll 1$

further if h_{oe} is omitted, the collector current I_c is given by $I_c = h_{fe} I_b$.

→ Under this condition the magnitude of voltage of generator in the emitter circuit is


$$h_{re} |V_c| = h_{re} I_c R_L = h_{re} h_{fe} I_b R_L.$$

Since $h_{re} h_{fe} \approx 0.01$

This voltage may be neglected in comparison with the voltage drop across $h_{ie} = h_{ie} I_b$

$$\begin{aligned} h_{re} &= 2.5 \times 10^{-4} \\ h_{fe} &= 50 \end{aligned}$$

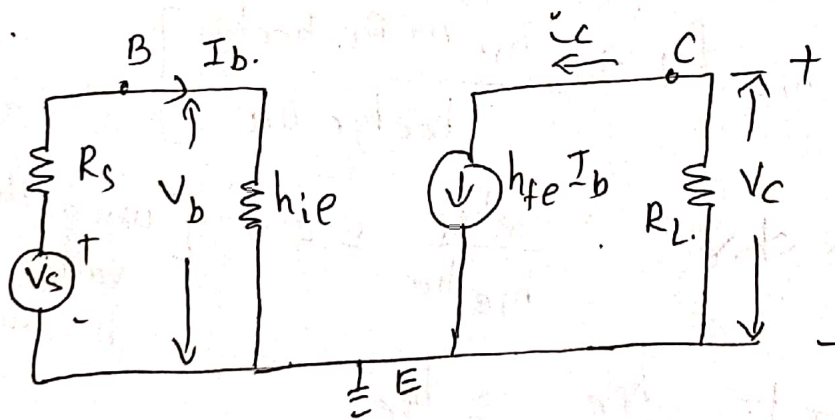→ To conclude, if the load resistance R_L is small it is possible to neglect the parameters h_{re} & h_{oe} and obtain the approximate equivalent circuit as shown.



→ Generalised Approximate model:

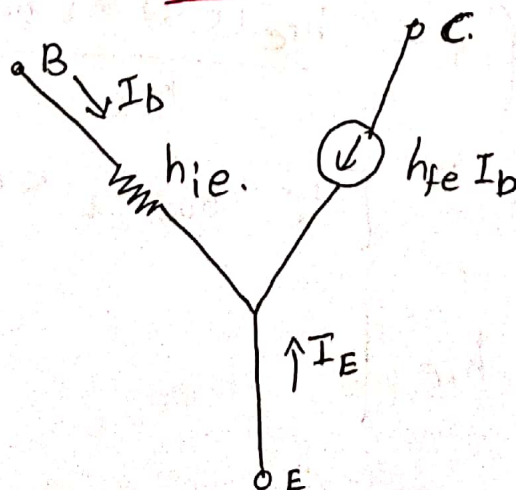


Figure shows the simplified hybrid circuit which can be used for any configuration by simply grounding the approximate terminal.

→ Analysis of CE configuration using approximate analysis:

(i) A_I = current gain:

$$\text{w.k.T} \quad A_I = \frac{-h_{fe}}{1 + h_{oe} R_L}$$

$$\text{if } h_{oe} R_L \ll 1 \Rightarrow h_{oe} R_L < 0.1$$

$$\boxed{A_I \approx -h_{fe}}$$

(ii) input impedance: Z_i or R_i :

$$\text{w.k.T} \quad R_i = h_{ie} + h_{re} A_I R_L$$

$$R_i = h_{ie} \left[1 + \frac{h_{re} A_I R_L h_{oe} h_{fe}}{h_{oe} h_{fe} h_{ie}} \right]$$

$$\approx h_{ie} \left[1 + \frac{h_{re} h_{fe}}{h_{ie} h_{oe}} \approx 0.5 \right] \quad \left[\text{using the typical values for the h-parameters} \right]$$

$$\text{further, } |A_I| = \frac{h_{fe}}{1 + h_{oe} R_L} \approx h_{fe}$$


$$R_i = h_{ie} \left[1 - \frac{h_{fe} (0.5) R_L h_{oe}}{h_{fe}} \right]$$

$$R_i \approx h_{ie} \quad \left[\because h_{oe} R_L < 0.1 \right]$$

$$\Rightarrow \boxed{R_i \approx h_{ie}}$$

Voltage gain $A_v = \frac{A_{\beta} R_L}{R_i}$
 $= \frac{-h_{fe} R_L}{h_{ie}}$

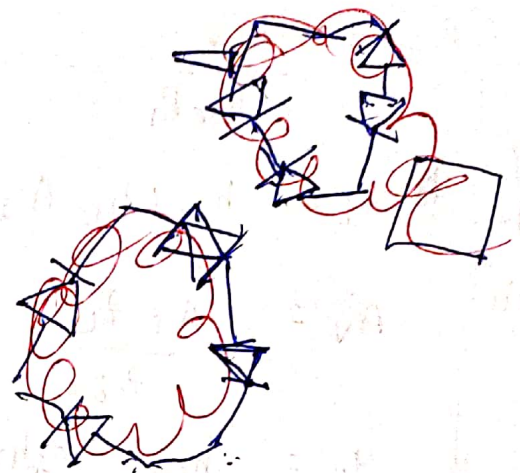
$\Rightarrow \boxed{A_v = \frac{-h_{fe} R_L}{h_{ie}}}$



output impedance:

It is the ratio of V_c to I_c with $V_s = 0$ & R_L excluded. The simplified circuit has infinite output impedance because with $V_s = 0$ & external voltage source applied at the output, it is found that $I_b = 0$ & hence $I_c = 0$.

$\Rightarrow \boxed{Z_o = \infty}$

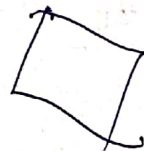

==

ii) \Rightarrow for a common emitter configuration using exact and approximate analysis is

using exact analysis	{	$A_I = \frac{-h_{fe}}{1+h_{oe}R_L}$	}	using approximate analysis	$A_I \approx -h_{fe}$
		$z_i = h_{ie} + h_{re} A_I z_L$			$z_i \approx h_{ie}$
		$A_V = \frac{A_I z_L}{z_i}$			$A_V \approx \frac{-h_{fe} z_L}{h_{ie}}$
		$Y_o = h_{oe} - \frac{h_{fe} h_{re}}{h_{ie} + R_s}$			$Y_o \approx 0$


iii) for common base configuration.

$A_I = \frac{-h_{fb}}{1+h_{ob}R_L}$	$A_I \approx -h_{fb}$
$z_i = h_{ib} + h_{rb} A_I z_L$	$z_i \approx h_{ib}$
$A_V = \frac{A_I z_L}{z_i}$	$A_V \approx \frac{-h_{fb} z_L}{h_{ib}}$
$Y_o = h_{ob} - \frac{h_{fb} h_{rb}}{h_{ib} + R_s}$	

iv) for common collector configuration:

$A_I = \frac{-h_{fc}}{1+h_{oc}R_L}$	$A_I \approx -h_{fc}$
$z_i = h_{ic} + h_{rc} A_I z_L$	$z_i \approx h_{ic}$
$A_V = \frac{A_I z_L}{z_i}$	$A_V \approx \frac{-h_{fc} z_L}{h_{ic}}$
$Y_o = h_{oc} - \frac{h_{fc} h_{rc}}{h_{ic} + R_c}$	

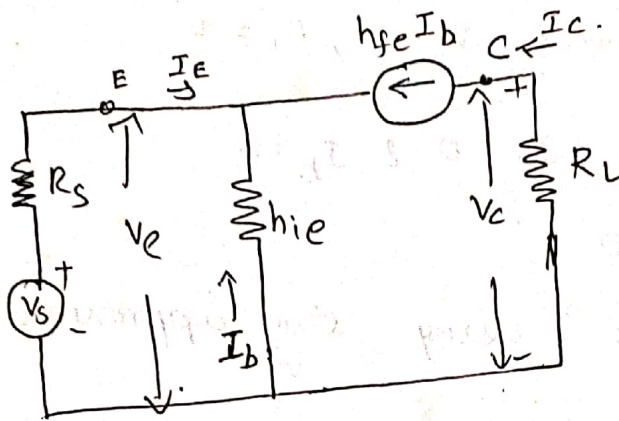Analysis of CB Amplifier using the approximate model:



Current gain:

$$A_I = \frac{-I_c}{I_e} = \frac{-h_{fe}I_b}{I_e}$$

$$A_I = \frac{-h_{fe}I_b}{-(I_b + h_{fe}I_b)} = \frac{h_{fe}I_b}{I_b(1+h_{fe})} = \frac{h_{fe}}{1+h_{fe}}$$

$$A_I = \frac{h_{fe}}{1+h_{fe}} = -h_{fb}$$

Input resistance:

$$R_i = \frac{V_e}{I_e}$$

$$= \frac{-I_b(h_{ie})}{-(1+h_{fe})I_b} = \frac{h_{ie}}{1+h_{fe}} = h_{ib}$$

$$R_i = h_{ib}$$

Voltage gain:

$$A_V = \frac{V_c}{V_e}$$

$$= \frac{-h_{fe}I_b R_L}{-I_b h_{ie}}$$

$$A_V = \frac{h_{fe} R_L}{h_{ie}}$$

output impedance:


$$R_o = \frac{V_c}{I_c} \quad \text{with } V_s = 0, R_L = \infty$$

$$\text{with } V_s = 0, I_e = 0 \text{ \& } I_b = 0$$

$$\text{hence } I_c = 0$$

Therefore, $R_o = \infty$ using the approximate model.

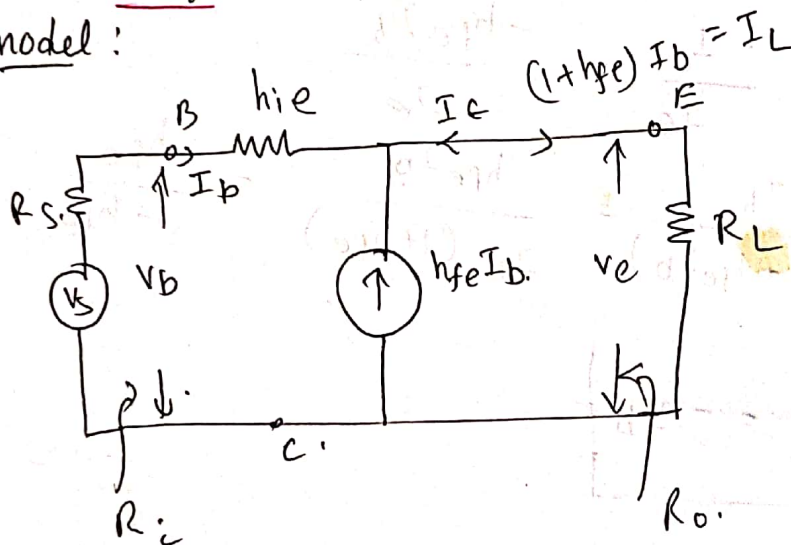⇒ Analysis of CC amplifier using the approximate model:



⇒ current gain (A_I):

$$A_I = \frac{I_L}{I_b} = \frac{(1+h_{fe}) I_b}{I_b} = (1+h_{fe})$$

$$\boxed{A_I = 1+h_{fe}}$$

⇒ input resistance: $z_i = \frac{V_b}{I_b}$

V_b from circuit

$$V_b = h_{ie} I_b + R_L (1+h_{fe}) I_b$$

$$z_i = \frac{[h_{ie} + R_L (1+h_{fe})] I_b}{I_b}$$

$$z_i = h_{ie} + R_L (1 + h_{fe})$$

Voltage gain:

$$\begin{aligned} A_v &= \frac{V_e}{V_b} = \frac{(1 + h_{fe}) I_b R_L}{[h_{ie} I_b + (1 + h_{fe}) I_b R_L]} \\ &= \frac{(1 + h_{fe}) R_L}{h_{ie} + (1 + h_{fe}) R_L} \\ &= \frac{h_{ie} + (1 + h_{fe}) R_L - h_{ie}}{h_{ie} + (1 + h_{fe}) R_L} \\ &= 1 - \frac{h_{ie}}{h_{ie} + (1 + h_{fe}) R_L} \end{aligned}$$

$$A_v = 1 - \frac{h_{ie}}{z_i}$$

Output impedance:


$y_o = \frac{I_L}{V_2}$ without R_L & $V_s = 0$.

w.k.T $I_L = (1 + h_{fe}) I_b$.

$$I_b = \frac{V_s}{h_{ie} + R_s}$$

$$I_L = \frac{(1 + h_{fe}) V_2}{h_{ie} + R_s}$$
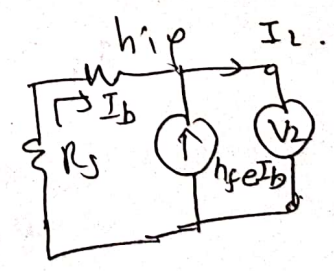
$$y_o = \frac{(1 + h_{fe}) V_2}{h_{ie} + R_s} / V_2$$



$$\Rightarrow y_o = \frac{1 + h_{fe}}{h_{ie} + R_s}$$

Comparison of h parameters:


Ans

$$h_{fc} = -(1+h_{fe}) \quad h_{ic} = h_{ie} \quad h_{ob} = \frac{h_{oe}}{1+h_{fe}}$$

$$h_{fb} = \frac{-h_{fe}}{1+h_{fe}} \quad h_{rc} = 1 \quad h_{oc} = h_{oe}$$

$$h_{ib} = \frac{h_{ie}}{1+h_{fe}} \quad h_{rb} = \frac{h_{ie}h_{oe} - h_{re}}{1+h_{fe}}$$

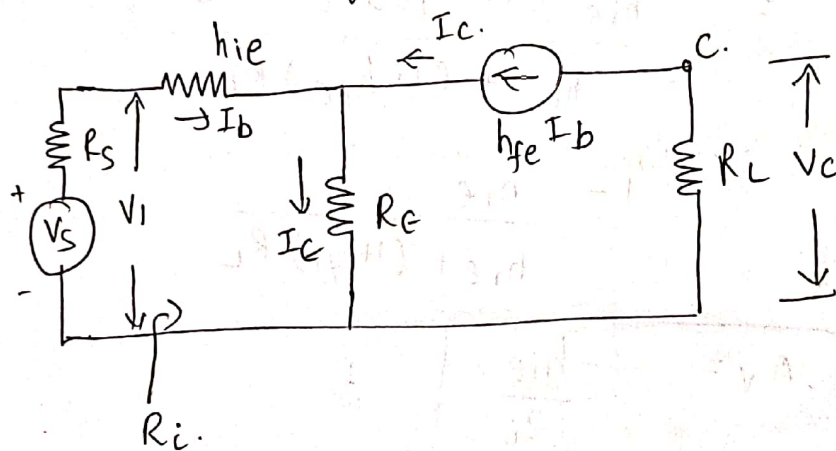→ Common emitter amplifier with emitter resistor:



$$A_I = \frac{I_L}{I_b} = \frac{-h_{fe} I_b}{I_b} = -h_{fe}$$

$$R_i = \frac{V_i}{I_b} = \frac{h_{ie} I_b + R_e (1+h_{fe}) I_b}{I_b}$$

$$R_i = h_{ie} + R_e (1+h_{fe})$$

Comparing $R_i = h_{ie}$ (without R_e), the input resistance is augmented by $(1+h_{fe})R_e$ & may be very much larger than h_{ie} .

Voltage gain (A_V):

$$A_V = \frac{A_I R_L}{R_i}$$

$$= \frac{-h_{fe} R_L}{h_{ie} + (1+h_{fe}) R_E}$$

Thus the addition of emitter resistor R_E greatly reduces the voltage amplification as R_i has increased from h_{ie} to $h_{ie} + (1+h_{fe}) R_E$.

Output resistance, R_o : $R_o = \infty$ with R_L included
 $R_o = R_L$ with R_L included

Q. A CE Amplifier is drawn by a voltage source of internal resistance $r_s = 800 \Omega$, & the load impedance is a resistance $R_L = 1000 \Omega$. The h parameters are $h_{ie} = 1k\Omega$, $h_{re} = 2 \times 10^{-4}$, $h_{fe} = 50$ & $h_{oe} = 25 \mu A/V$. Compute A_I , A_V , R_i , & R_o using exact & approximate analysis.

Ans

$$A_I = \frac{-h_{fe}}{1 + h_{oe} R_L} = -48.78$$

$$A_I = -h_{fe} = -50$$

$$R_i = h_{ie} - \frac{h_{fe} h_{re}}{h_{oe} + \frac{1}{R_L}} = 990.24 \Omega$$

$$R_i = h_{ie} = 1k\Omega$$

$$A_V = \frac{A_I R_L}{R_i} = -44.26$$

$$A_V = \frac{-h_{fe} R_L}{R_{ip}} = -50$$

$$R_o = \frac{1}{Y_o} \Rightarrow Y_o = h_{oe} - \frac{h_{fe} h_{re}}{h_{ie} + R_s}$$


$$= 1.94 \times 10^{-5} S$$

$$R_o = 51.42 k\Omega$$


$$R_o = \infty$$

Q For the circuit shown below find A_I , A_V , R_i & R_o using approximate model
 $\beta_{fe} = 100$, $h_{ie} = 2\text{ k}\Omega$, $I_b = 100\mu\text{A}$.

Ans

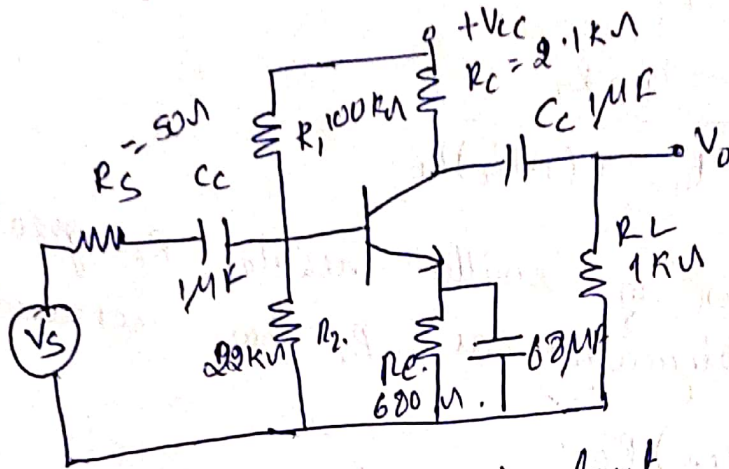

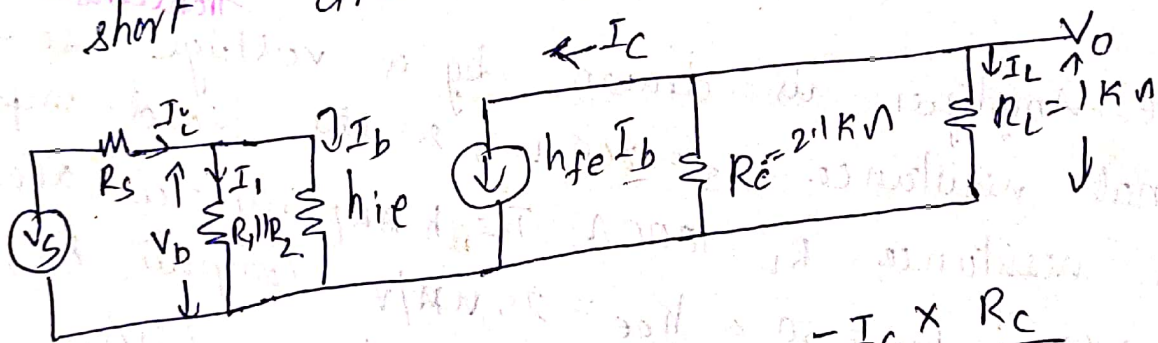→ Draw the ac equivalent circuit for this, $V_{CC} = 0\text{V}$ or GND, capacitor acts as short circuit for a test frequency.



$$A_I = \frac{I_L}{I_i} = \frac{I_L}{I_1 + I_b}$$

$$I_L = -I_C \times \frac{R_C}{R_C + R_L}$$

$$I_L = -\frac{\beta_{fe} I_b R_C}{R_C + R_L} = -6.78\text{ mA}$$

$$I_1 = \frac{V_b}{R_1 || R_2}$$

$$V_b = h_{ie} I_b = 0.2\text{ V}$$

$$I_1 = \frac{0.2}{R_1 || R_2} = 4\mu\text{A}$$

$$\Rightarrow A_I = \frac{-6.78\text{ mA}}{4\mu\text{A} + 100\mu\text{A}} = -65 \Rightarrow \boxed{A_I = -65}$$

$$R_i = \frac{V_b}{I_i} = \frac{h_{ie} I_b}{I_{\cancel{b}} + I_b} = \frac{2K \times 100\mu}{4\mu + 100\mu}$$

$$\boxed{R_i = 1.8K\Omega}$$

or $R_i = h_{ie} \parallel R_1 \parallel R_2$

$$A_v = \frac{V_c}{V_b} = \frac{I_L R_L}{h_{ie} I_b} = \frac{-0.78m \times 1K\Omega}{2K \times 100\mu}$$

$$\boxed{A_v = -33.9}$$

o/p impedance : $R_o = R_c$ without R_L
 $R_o = R_c \parallel R_L$ with R_L