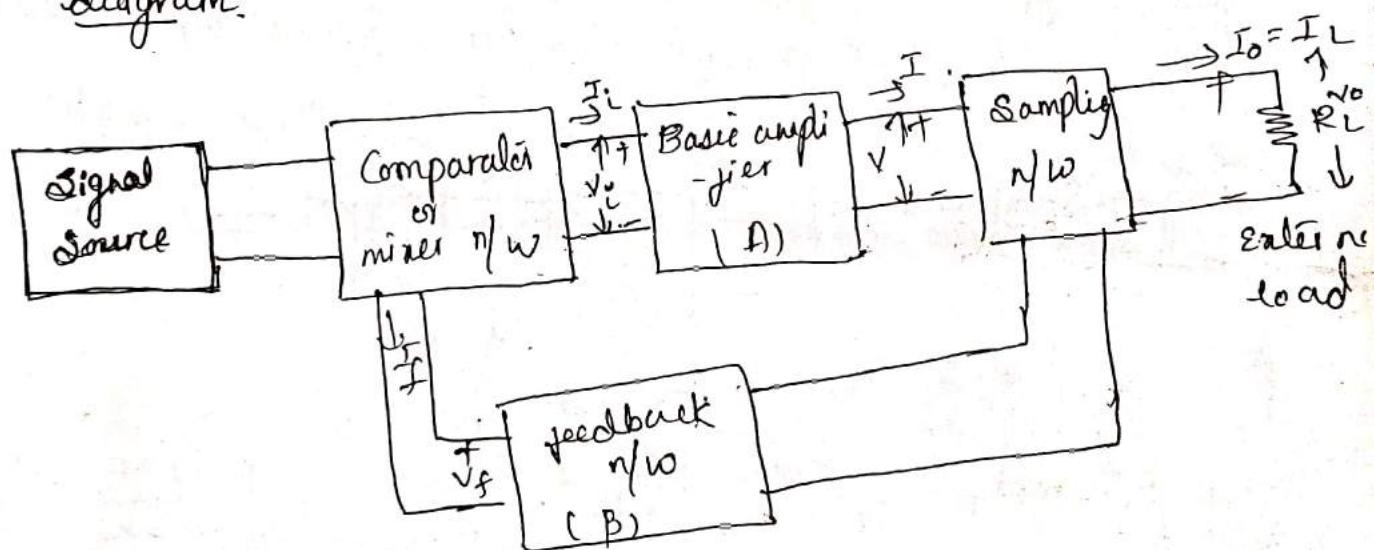


Feedback Concept:

Feedback is defined as some part of the output is added or subtracted with the input through a feedback network is called as feedback. Feedback amplifiers are used when the magnitudes of impedances at input and output are to be varied. The four basic amplifiers changing can be used as a feedback amplifiers.

Block diagram:



In the four basic amplifier circuits we may sample the o/p voltage or current by mean of a suitable sampling n/w and apply this signal to the input through a feedback two-port n/w.

At the input the feedback signal is combined with the external signal (source) through a mixer n/w and is fed into the amplifier properly.


Feedback Concept:

Feedback is defined as some part of the output is added or subtracted with the input through a feedback network is called as feedback.

Feedback amplifiers are used when the magnitudes of impedances at input and output are varied.

The four basic amplifiers with their impedances can be used as a feedback amplifiers.

Block diagram:

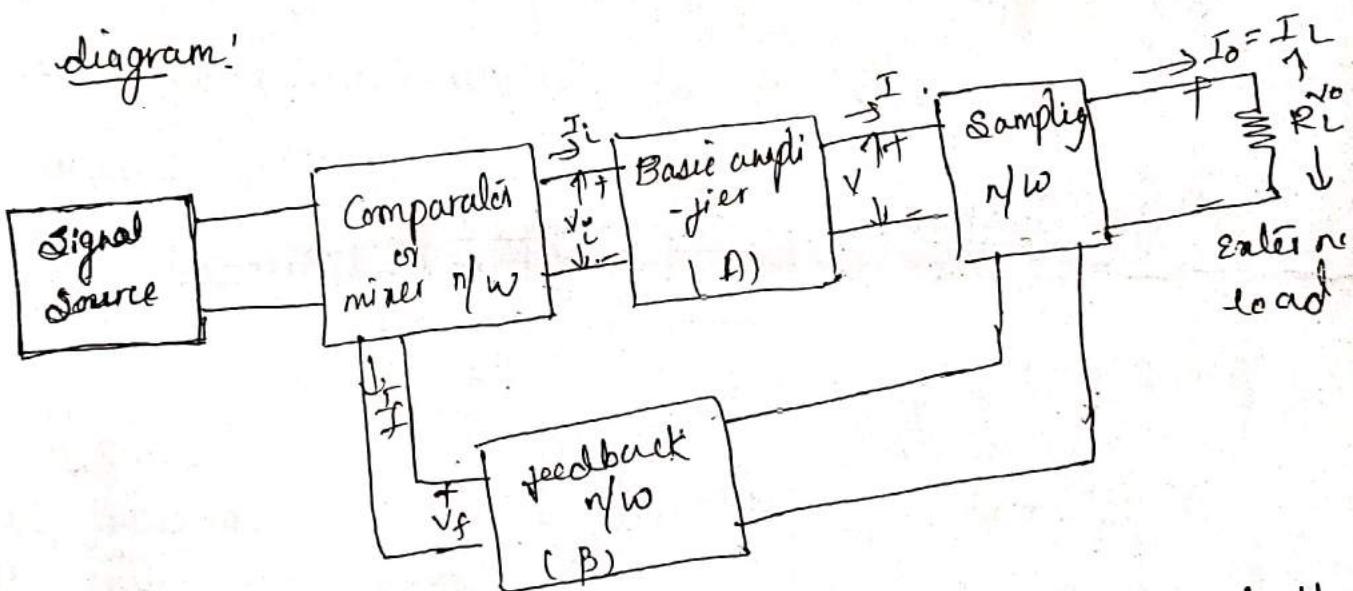

In the four basic amplifier circuits we may sample the o/p voltage or current by mean of a suitable sampling n/w and apply this signal to the input through a feedback two-pole n/w.

At the input the feedback signal is combined with the external signal (source) through a mixer n/w and is fed into the amplifier properly.

Signal Source: This block is either a signal series with a resistor R_s (a Thévenin representation) or a signal current I_s in parallel with a resistor R_s (a Norton representation).


Feedback Network: This block is usually a passive 2-port n/w which may contain resistors, capacitors and inductors. It is simply a resistive configuration.

Sampling Network:

Two types:

1. Voltage Sampler \rightarrow means o/p voltage is fed c/p
2. Current Sampler \rightarrow means o/p current is fed i/p.


Voltage Sampler:

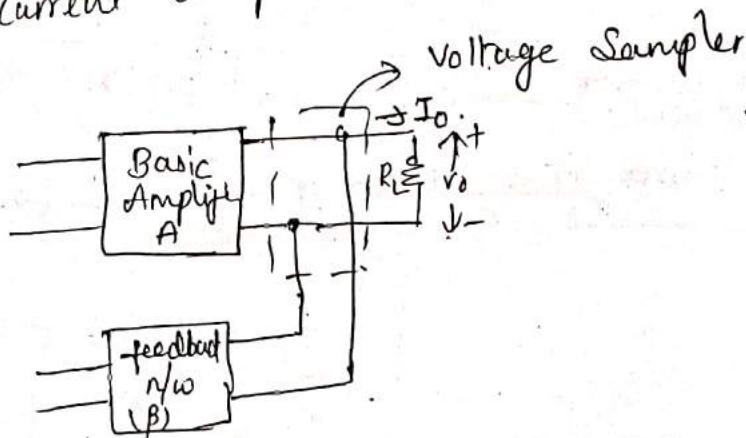

The output voltage is sampled by connecting the feedback n/w in shunt across the output. This type of connection is referred to as voltage or node sampling.

Current Sampler:

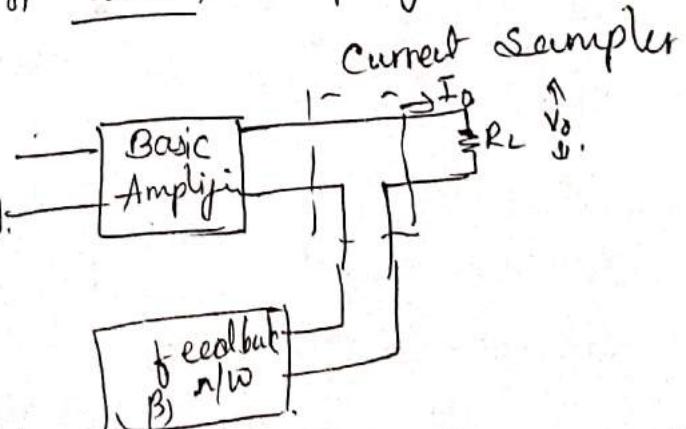The output current is sampled where the feedback n/w is connected in series with the output. This type of connection is referred to as current or loop sampling.



Comparison or Mixer n/w:

A comparison or mixer where the feedback output is mixed with input source.

Two types of mixers:


1. Series Mixing

2. Shunt Mixing

Series mixing: The feed back output from the feedback signal source.

n/w is in series with the

There fore the signal source in

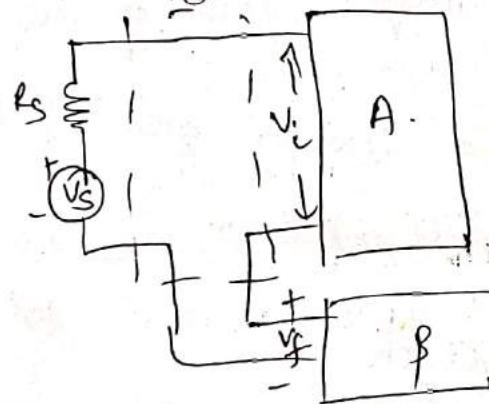

is thevenine source.


Series mixing the
o/p of the feedback n/w
is voltage.

Shunt Mixing:

The feedback output from the feedback n/w is in shunt with its signal source.

Therefore, the signal source is a Norton source.

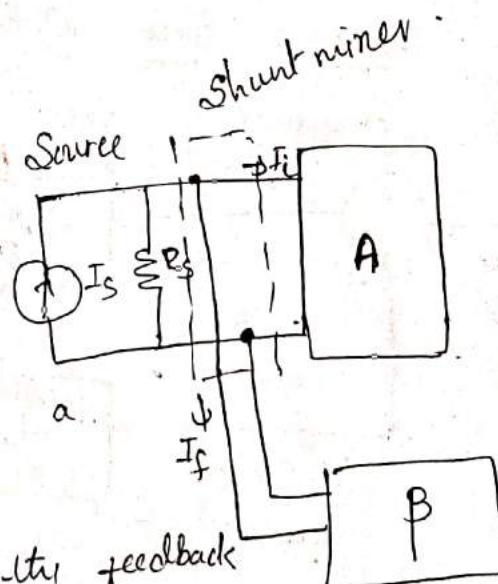In shunt mixing the o/p of the feedback n/w is current.



Transfer Ratio; or Gain

The symbol A represents the ratio of the output signal to the input signal of the basic amplifier. The transfer ratio V_o/V_i is the voltage gain A_v . If I_o/I_i is the current amplification or current gain A_I , for the amplifier.


The ratio I_o/V_i of the amplifier is the transconductance G_m .

V_o/I_i is the trans-resistance R_M .

→ A_v, A_I, G_m , & R_M as a transfer gain of the basic amp without feedback.

→ A_{vf}, A_I, G_m & R_M as a transfer gain of the amplifier with feedback.

The Transfer Gain with feedback

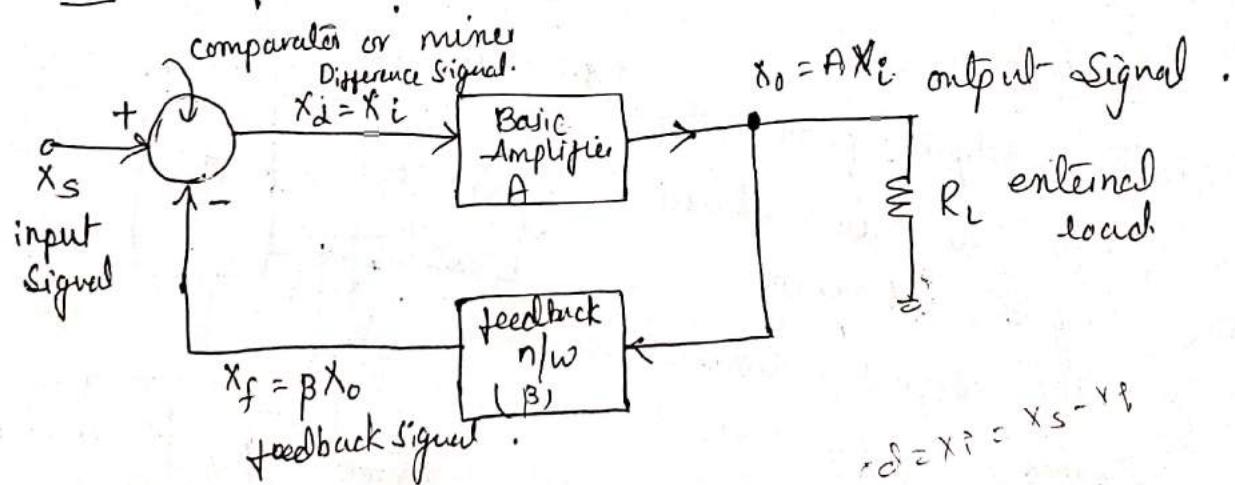

$$\text{from fig: } x_d = x_i = x_s - x_f$$

$$\text{feedback factor } \beta = \frac{x_f}{x_o} \Rightarrow x_f = x_o \beta$$

transfer gain

$$A = \frac{x_o}{x_i}$$

$$x_d = x_i = x_s - x_f$$

(4)

The gain A_f of feedback $A_f = \frac{X_o}{X_s}$

$$A_f = \frac{X_o}{X_i + X_f} \quad [\text{from } X_o = X_s - X_f]$$

$$A_f = \frac{X_o}{X_i + \beta X_o}$$

Divide NR & DR by X_i


$$A_f = \frac{X_o/X_i}{1 + \beta \frac{X_o}{X_i}}$$

w.k.t $\frac{X_o}{X_i} = A$

$$A_f = \frac{A}{1 + A\beta}$$

→ Types of feedback amplifiers!

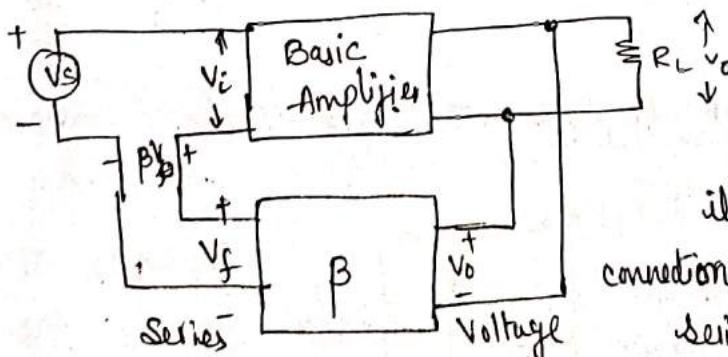↳ Voltage Series feedback amplifier or,
voltage amplifier with voltage series feedback




☞ Voltage Series
means o/p shunt
or node connection as
it is voltage and o/p series
connection or voltage source as it is
series mixing.

→ o/p to the feedback n/w is voltage and $\frac{\text{feedback}}{\text{voltage}}$ is added at o/p

$$\beta = \frac{V_f}{V_o}; \quad A_v = \frac{V_o}{V_i}$$

$$A_{vf} = \frac{V_o}{V_s}$$

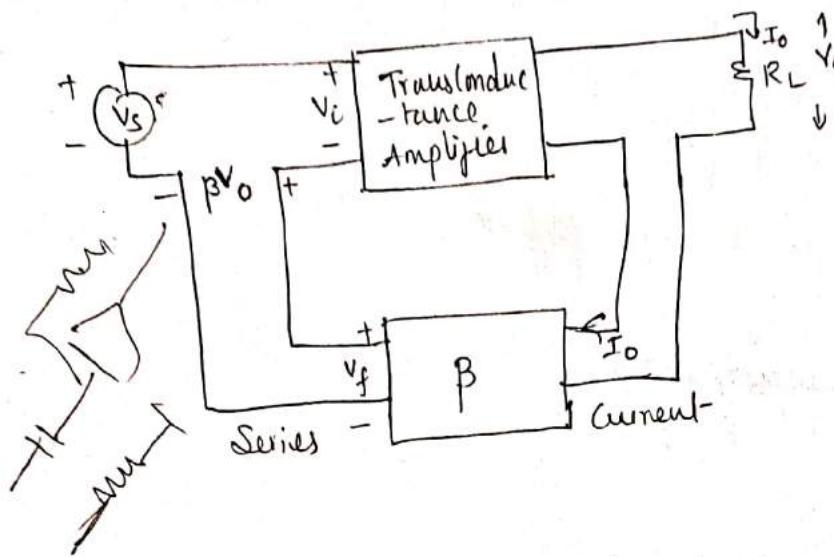3. Current Series feedback amplifier or
amplifier with current series feedback.




of.

$$\beta = \frac{V_f}{I_o}$$

$$G_M = \frac{I_o}{V_i}$$

$$G_{M_f} = \frac{I_o}{V_s}$$

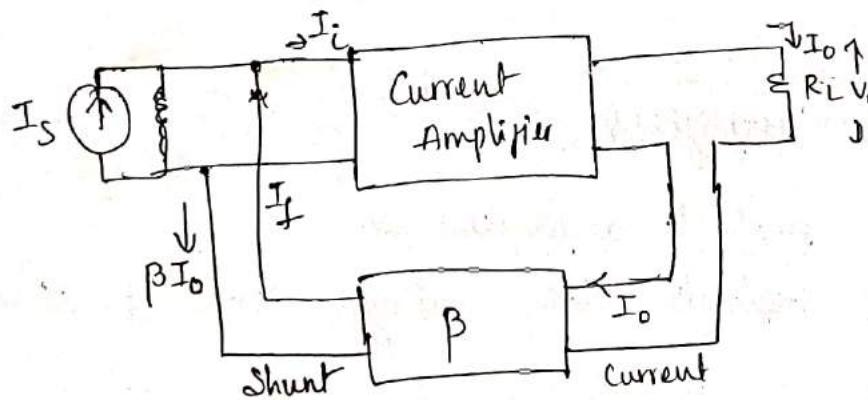3. Current Amplifier with current shunt feedback or current shunt feedback amplifier.




$$\beta = \frac{I_f}{I_o}$$

$$A_I = \frac{I_o}{I_i}$$

$$A_{If} = \frac{I_o}{I_s}$$

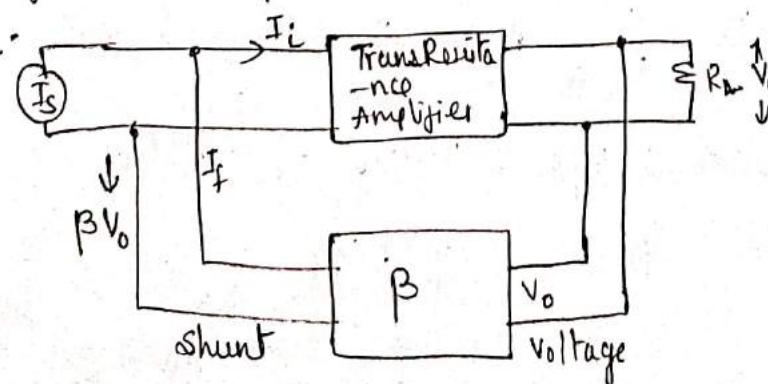4) Voltage Shunt feedback Amplifier (or) Transresistance Amplifier with voltage shunt feedback:



$$\beta = \frac{I_f}{V_o}$$

$$R_M = \frac{V_o}{I_i}$$

$$R_{M_f} = \frac{V_o}{I_s}$$

Signal or Ratio	Voltage Series	Current Series	Current Shunt	Voltage shunt
X_o (Colp)	Voltage	Current	Current	Voltage
X_s, X_f, X_d	Voltage	Voltage	Current	Current
A	A_v	G_m	A_I	R_M
P	V_f/V_o	V_f/I_o	I_f/I_o	I_f/V_o

ADVANTAGES OF NEGATIVE FEEDBACK:

1. Stability of gain
 2. Reduction in Distortion
 3. Reduction in Noise
 4. Increased Bandwidth
 5. Increased input impedance
 6. Decreased output-impedance.
1. Gain Stabilization:
The gain of an amplifier may change because of so many reasons. change in power supply voltage, or change in the parameters of the active device (FET or transistor) may change the gain.

This adversely effects the performance of the amplifier. It would have been ideal, if the gain of the amplifier was independent of these changes.

Negative feedback achieves this object to a great extent.
The gain of a negative feedback amplifier is given.

as

$$A_f = \frac{A}{1 + A\beta}$$

but $A\beta \gg 1$, then in denominator unity can be neglected compared to $A\beta$

$$\therefore A_f = \frac{A}{A\beta} = \frac{1}{\beta}$$

$$\boxed{A_f = \frac{1}{\beta}}$$

- Thus, the gain A_f of the feedback amplifier is made independent of the internal gain A .
- The gain A_f depends only on β which in turn depends on passive elements such as resistors.
- The values of the resistors remain fairly constant and hence the gain is stabilized.
- Even if $A\beta \gg 1$ condition is not fully met, some improvement occurs in the stability of the gain.
- Suppose a certain change in the internal gain of the amplifier takes place. we can find the corresponding % change in the overall gain of the feedback amplifier.

w.r.t $A_f = \frac{A}{1 + A\beta}$ Ans

Differentiating w.r.t A

$$\frac{dA_f}{dA} = \frac{(1+A\beta) \times (1) - A\beta}{(1+A\beta)^2}$$

$$\frac{dA_f}{dA} = \frac{1}{(1+A\beta)^2} \Rightarrow \frac{dA_f}{dA} = \frac{1}{1+A\beta} \times \frac{1}{1+A\beta}$$

$$\frac{dA_f}{dA} = \frac{A_f}{A} \times \frac{1}{1+A\beta} \quad \left\{ \because \frac{1}{1+A\beta} = \frac{A_f}{A} \right\}$$

$$\boxed{\frac{dA_f}{A_f} = \frac{1}{(1+A\beta)} \frac{dA}{A}} \quad \text{--- (1)}$$

since $(A\beta + 1) > 1$, the % change in A_f is seen to be much less than the % change in A .

Desensitivity: It can be defined as change in voltage gain without feedback to the change in voltage gain with feedback.

$$D = (1+A\beta) = \frac{\frac{dA}{A}}{\frac{dA_f}{A_f}} \quad [\text{from (1) equation}]$$

Sensitivity: It is defined as inverse of desensitivity ratio of change in voltage gain with feedback to the change in voltage gain without feedback

$$S = \frac{1}{1+A\beta} = \frac{\frac{dA_f}{A_f}}{\frac{dA}{A}}$$

Reduction in Distortion & Noise:

In negative feedback the harmonic distortion is reduced.

This can be shown as:

→ v_f is distorted since o/p of amplifier is distorted.

• A flattened o/p when subtracted from its o/p becomes a resulting o/p v_o' of more peaked.

→ Thus the net o/p v_o' is pre-distorted in such a way so as to partially compensate for the flattening caused by v_i at the amplifier.

→ we can find the amount of reduction in the distortion caused by -ve feedback.

Suppose the amplifier with gain A produces a distortion D without feedback.

After f/b applied this distortion D appears as D_f .



D_f gets multiplied with β and βD_f part of distortion D_f is fed back to the input.

This gets amplified A times by the basic amplifier and becomes $A \beta D_f$. This gets added up (in reverse polarity) to the original distortion D to make the net distortion D_f , Thus

$$D_f = D - A \beta D_f$$

$$D_f = \frac{D}{1 + A \beta}$$

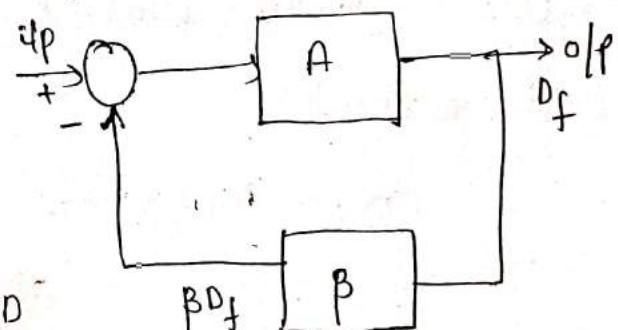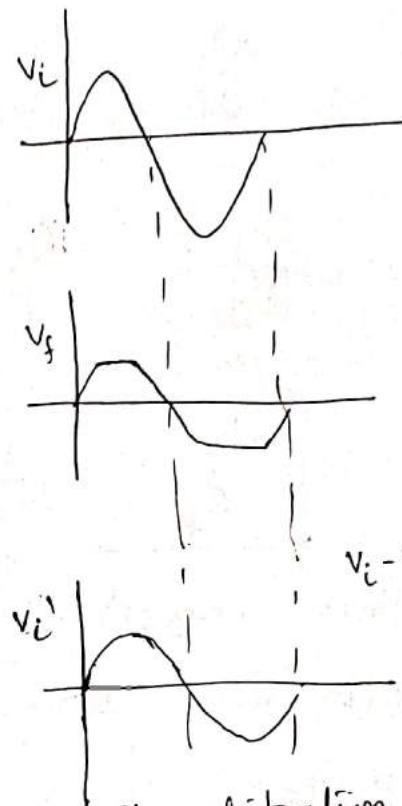The distortion is reduced by the same factor as gain



$$\text{By Noise } N_f = \frac{N}{1 + A\beta}$$

④ Increased Bandwidth:

- W.K.T due to -ve f.b the gain is reduced by a factor of $(1 + A\beta)$.
- also negative feedback reduces the f_1 lower cut off frequency by a factor of $(1 + A\beta)$ & f_2 higher cut off freq by a factor of $(1 + A\beta)$

but $BW_f = f_2 - f_1$
as $f_2 \gg f_1$

$$∴ BW_f \approx f_2$$


i. Bandwidth increases by a factor of $(1 + A\beta)$

$$⇒ \boxed{BW_f = BW(1 + A\beta)}$$

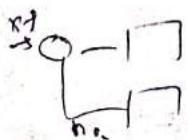ii. $f_{L_f} \rightarrow$ lower cut off frequency with feedback:

w.k.t $A_{V_L} = \frac{AV_m}{1 - j\left(\frac{f_L}{f}\right)}$ [gain in LFR]

$A_{V_f} = \frac{A_{V_L}}{1 + A_{V_L}\beta}$ [in the form of $A_f = \frac{A}{1 + A\beta}$]
gain in LFR with feedback



$$A_{V_f} = \frac{\frac{AV_m}{1 - j\left(\frac{f_L}{f}\right)}}{1 + \left(\frac{AV_m}{1 - j\left(\frac{f_L}{f}\right)}\right)\beta}$$

$$1 + \left(\frac{AV_m}{1 - j\left(\frac{f_L}{f}\right)}\right)\beta$$

$$AV_{L_f} = \frac{\frac{AV_m}{1-j\left(\frac{f_L}{f}\right)}}{\frac{1-j\left(\frac{f_L}{f_0}\right) + AV_m\beta}{\left[1-j\left(\frac{f_L}{f}\right)\right]}}$$

$$\Rightarrow AV_{L_f} = \frac{AV_m}{1-j\left(\frac{f_L}{f_0}\right) + AV_m\beta}$$

taking $(1 + AV_m\beta)$ common.

$$AV_{L_f} = \frac{\frac{AV_m}{1+AV_m\beta}}{1 - j \frac{f_L}{f_0(1+AV_m\beta)}}$$

$$AV_{L_f} = \frac{AV_{m_f}}{1 - j \frac{f_L}{f_0(1+AV_m\beta)}} \quad \left[\because AV_{m_f} = \frac{AV_m}{1+AV_m\beta} \right]$$

gain w.r.t. b in midband region

$$AV_{L_f} = \frac{AV_{m_f}}{1 - j \left(\frac{f_{L_f}}{f} \right)} \quad \text{where } f_{L_f} = \frac{f_L}{1+AV_m\beta}$$

$$\Rightarrow f_{L_f} = \text{lower cutoff freq with feedback} = \frac{f_L}{1+AV_m\beta}$$

reduces by a factor of $(1 + AV\beta)$

(ii) $f_{H_f} = f_H (1 + AV_m\beta) \Rightarrow$ increases by a factor of $(1 + AV\beta)$

⑤ Increased input Impedance:

2, 20, 36, 52, (8)
④ ⑤

It is desirable to have a high input impedance for an amplifier.

Then it will not load the preceding stage or the input voltage source. Such a desirable characteristic can be achieved with the help of negative or series voltage feedback.

$$R_{if} = R_i (1 + A\beta)$$

The input impedance is increased by a factor of $(1 + A\beta)$.

⑥ Decrease in output impedance:

Low impedance at o/p is advantageous for an amplifier.

An amplifier with low impedance is capable of delivering power (or voltage) to the load without much loss.

Such a desirable characteristic is achieved by employing negative series-voltage feedback in the amplifier.

$$R_{of} = \frac{R_o}{1 + A\beta}$$

The output impedance is reduced by a factor of $(1 + A\beta)$.

METHOD OF ANALYSIS OF A FEEDBACK AMPLIFIER

① Analysis of feedback amplifiers involves determination of the four parameters, namely voltage gain, current gain, input impedance and output impedance of the amplifier with feedback.

In order to determine these parameters, the type of the circuit, the type of feedback involved in the circuit, the transfer ratio of the amplifier without feedback is to be established. With the help of these parameters the analysis of the amplifier can be performed.

The analysis of any type of feedback amplifier can be consolidated as following steps:

① Redraw the ckt and identify the active devices and its terminals.

② Identify the topology

a) Is the feedback signal x_f a voltage or current?

In other words, is x_f applied in series or in shunt with the external excitation?

b) Is the sampled signal x_o a voltage or current?

In other words, is the sampled signal taken at the off node or from the o/p loop?

③ Draw the ckt of the amplifier without feedback by using following steps:

a) To find the input ckt

set $V_o = 0$ for voltage sampling / short the o/p node

set $I_o = 0$ for current sampling / open the o/p loop

b) To find its output ckt

Set $V_i = 0$ for shunt comparison / short the clip node

Set $I_i = 0$ for series comparison / open the clip drop

- (4) Use a Thvenen's source if x_f is a voltage or
Norton's source if x_f is a current
- (5) replace each active device by its appropriate equivalent model.
6. By applying KCL & KVL to the equivalent circuit
determines the transfer ratio A of the amplifier with
feedback

7. Indicate x_f & x_o in the ckt & evaluate β rat


8. From the values of A & β , find D , A_f , R_{if} & R_o

61

85, 91, 104, 110

112, 113, 131

PROBLEMS

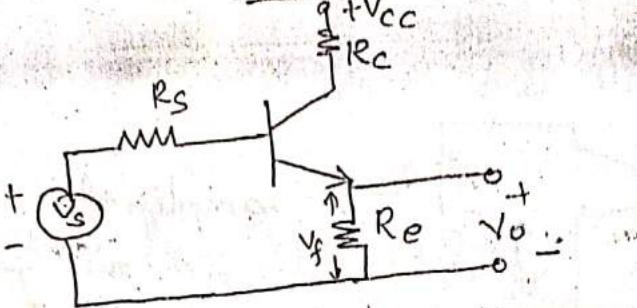

i. Identifying the topology:

as the feedback element is R_E
As R_E is not connected directly to the input
terminal base it is a series mixing.

or

as the feedback output is voltage seri.
series mixing.

b. as $A = V_f \propto V_o$

$$\text{or } V_f = I_e R_E$$

$$\text{or } V_f \text{ where } I_e R_E = V_o$$

$$\therefore V_f \approx V_o$$

$$\text{or } V_f \propto V_o$$


∴ voltage sampling

⇒ voltage series amplifier

ii. i/p loop:


for drawing i/p loop of this amplifier
set $V_o = 0$ [as voltage sampling]

Ckt becomes \Rightarrow

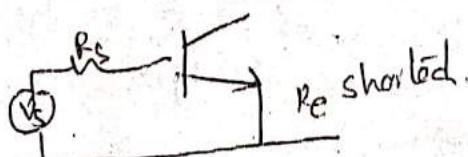


for o/p loop set $I_i = 0$ [for series mixing]

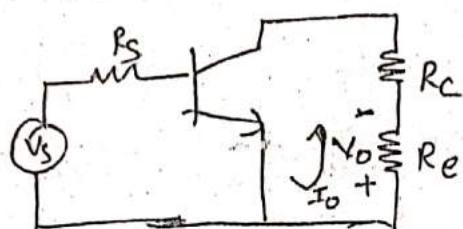Signal from o/p to i/p from β n/w is zero.



amplified circuit
with out feedback

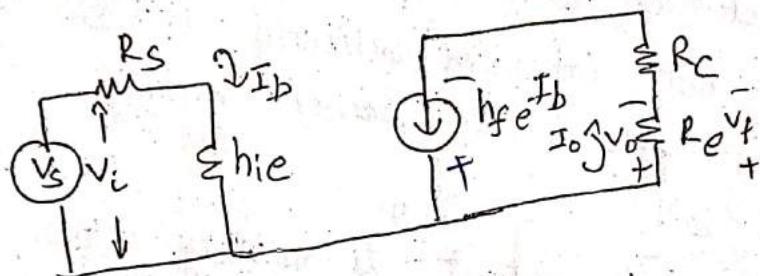iii. Replacing transistor by approximate model.



$$\beta = \frac{V_f}{V_o} = 1$$

$$V_i = V_s = (h_{ie} + R_s) I_b$$

$$A_v = \frac{V_o}{V_i}$$

or

$$V_o = h_{fe} I_b R_e$$

$$\rightarrow A_v = \frac{h_{fe} I_b R_e}{(h_{ie} + R_s) I_b} = \frac{h_{fe} R_e}{h_{ie} + R_s}$$

$$A_v = \frac{h_{fe} R_e}{h_{ie} + R_s}$$

$$\rightarrow D = 1 + A_v \beta = 1 + A_v = 1 + \frac{h_{fe} R_e}{h_{ie} + R_s}$$

$$\rightarrow A_{vf} = \frac{A_v}{D}$$

$$\rightarrow R_{vf} = R_i D \Rightarrow R_i = h_{ie} + R_s$$

$$\rightarrow R_{of} = \frac{R_o}{1 + A_v \beta} \Rightarrow$$

$R_{of} \rightarrow$ o/p impedance without R_L

To find o/p impedance open R_E and connect V with current I

for looking from open R_E

$$f_0 \rightarrow \infty$$


$\therefore R_{of} \rightarrow \infty$ as it is indetermined value so we have to find R_{of} then find R_{of} .

$$R_{of}' = R_O || R_E$$

$$R_{of}' \approx R_E$$

$$R_{of}' = \frac{R_o'}{D} = \frac{R_E}{D} = \frac{R_E(R_s + h_{ie})}{R_s + h_{ie} + h_{fe} R_E}$$
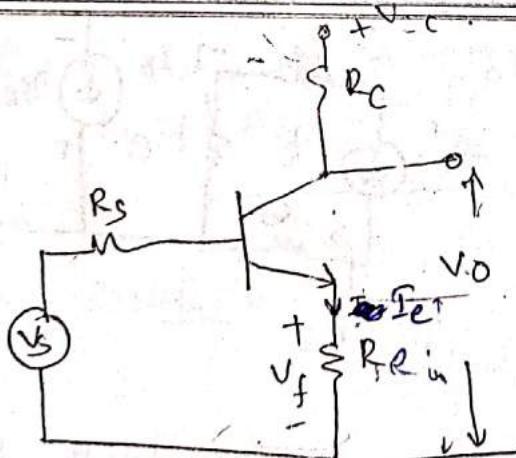
$$R_{of} = \underset{R_E \rightarrow \infty}{\text{ut}} R_{of}' = \frac{R_s + h_{ie}}{\frac{R_s + h_{ie}}{R_E} + h_{fe}} = \frac{R_s + h_{ie}}{h_{fe}}$$



i) Identifying the topology
ii) as feedback resistor R_F is not connected to base series mixing.

or
as feedback o/p is V_f .
series mixing.

iii) $V_f = R_E I_E$

$$I_E \approx I_o$$


$$V_f = R_E I_o$$

$V_f \propto I_o$ as V_f is proportional to o/p current.

$V_f \propto I_o$ as V_f is proportional to o/p current.
current sampling \therefore Current Series Amplifier


3 i/p loop

$I_o = 0$ [as current sampling]

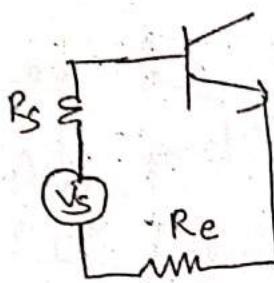


3 o/p loop

$I_i = 0$ (as series mixing).

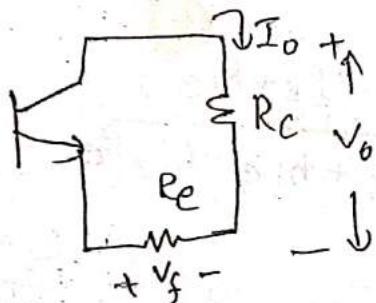

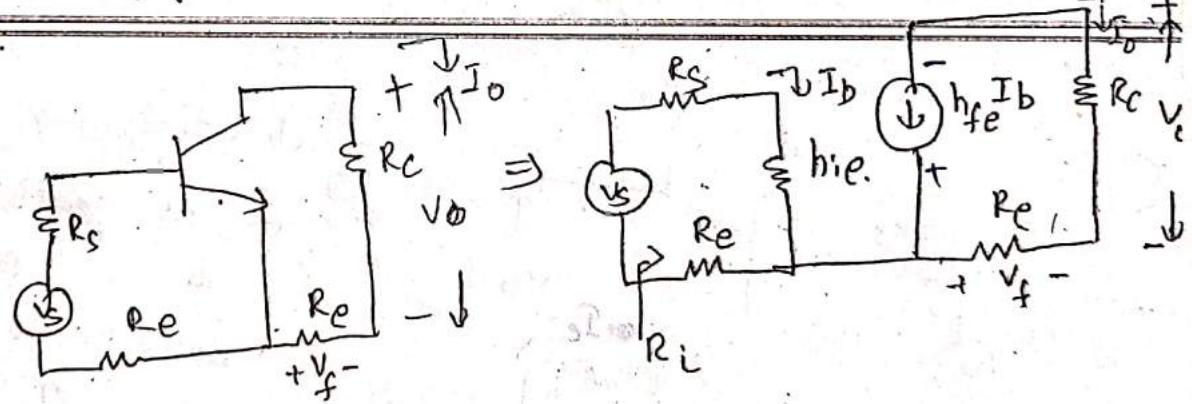④ The amplified ckt w.o.f.b. and with approximate model.



$$V_f = -I_o R_e$$

$$\beta = \frac{V_f}{I_o} = \frac{-I_o R_e}{I_o} = -R_e$$

$$\boxed{\beta = -R_e}$$

$$V_s = (R_s + h_{ie} + R_e) I_b$$

$$G_M = \frac{I_o}{V_s} = \frac{I_o}{V_L}$$

$$I_o = -h_{fe} I_b$$

$$G_M = \frac{-h_{fe}}{R_s + h_{ie} + R_e}$$

$$D = 1 + G_M \beta = 1 + \frac{h_{fe} R_e}{R_s + h_{ie} + R_e}$$

$$D = \frac{R_s + h_{ie} + R_e + h_{fe} R_e}{R_s + h_{ie} + R_e}$$

$$\begin{aligned} G_{Mf} &= \frac{G_M}{D} = \frac{-h_{fe}}{(R_s + h_{ie}) + R_e(1 + h_{fe})} \\ &= \frac{-h_{fe}}{R_e h_{fe}} \approx -\frac{1}{R_e}. \end{aligned}$$

To calculate voltage gain.

$$A_{Vf} = \frac{V_o}{V_s} = \frac{I_o R_c}{V_s} = G_{Mf} R_c.$$

$$A_{Vf} = -\frac{R_c}{R_e}$$

$$\text{Input Resistance: } R_{if} = R_i D$$

$$R_i = (R_s + h_{ie} + R_e)$$

Output resistance:

$$R_{of} = R_o (1 + G_m \beta).$$


R_o to find open R_c .

$$R_o = \infty \Rightarrow R_{of} = \infty$$

$$R_{of}' = R_{og} (1 + G_m \beta) R_L / R_{of} \quad \because \text{with } R_L$$

$$R_o' = R_o \parallel R_c \approx R_c$$

$$R_{of}' = R_c (1 + G_m \beta)$$

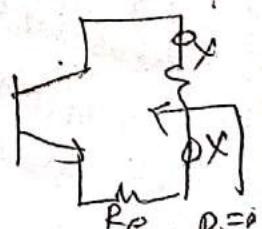


$$R_{of}' = R_o (1 + \beta G_m) / (1 + \beta G_m)$$

G_m neps shortcircuited transconductance

$$\text{Then } G_m = \frac{I_o}{R_L} \rightarrow G_m$$

from G_M equ
it is indep of
 R_L & hence
 $G_m = G_M$
& $R_{og}' = R_o' = R_L$
 R_c
where $R_o' = R_o \parallel R_c$
 $\approx R_c$.

(3)

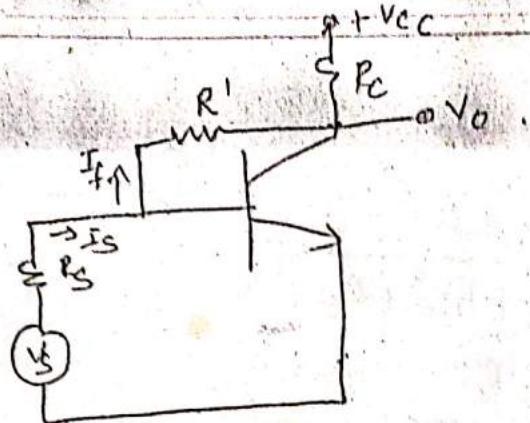

In identifying the topology, it is identified that feedback resistor R'_f is connected directly to the base. This is shunt sampling or signal. The feedback o/p is I_f .

ii,

$$I_f = \frac{V_i - V_o}{R'_f} \approx \frac{-V_o}{R'_f}$$

Since V_i is in mV for ampl. when compared to V_o which is in volts $V_o \gg V_i$

$$I_f \propto V_o$$

As $I_f \propto V_o$ it is voltage sampling


\therefore voltage shunt feedback amplifier.

3 o/p loop:



set $V_o = 0$ [as voltage sampling]

3 o/p loop


Set $V_i = 0$ (as shunt sampling)

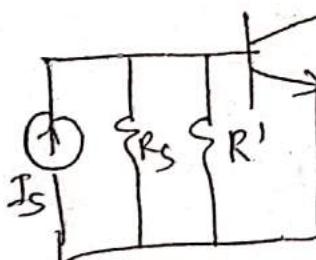

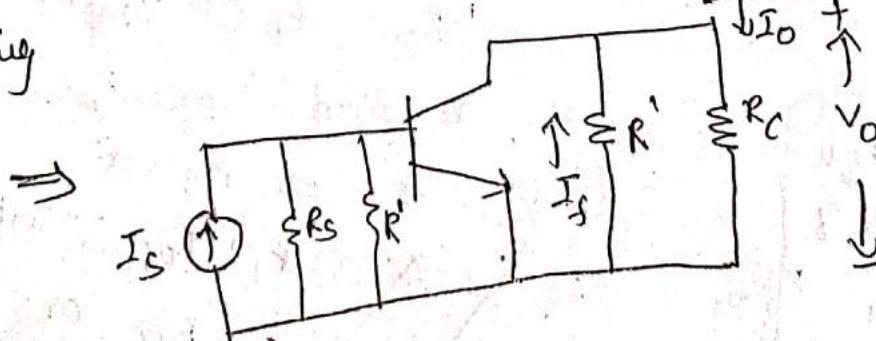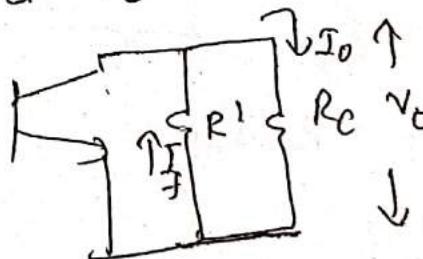Replacing thevenin of o/p as
Norton's
 \therefore shunt sampling



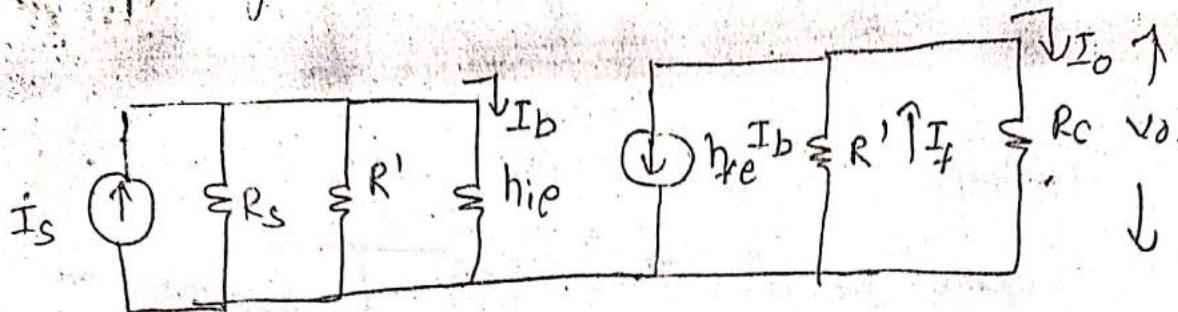Replacing Transistor with an approximate model



$$\beta = \frac{I_f}{V_o} = \frac{I_f}{-R' I_f} = -\frac{1}{R'}$$


$V_o = I_o R_C$
or
 $V_o = -R' I_f$

$$\boxed{\beta = -\frac{1}{R'}}$$

$$R_M = \frac{V_o}{I_i} = \frac{V_o}{I_S}$$

$$= \frac{-h_{fe} I_b \times R_L}{I_S}$$

$$R_L = R' \parallel R_C$$

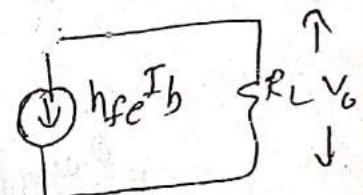

$$R_L = R' \parallel R_C$$

$$I_b = I_S \times \frac{R}{R + h_{ie}} \quad \text{where } R = R_S \parallel R'$$

$$I_S = I_b \frac{(R + h_{ie})}{R}$$

$$R_M = \frac{-h_{fe} R_L I_b \times R}{I_b (R + h_{ie})} = \frac{-h_{fe} R_L R}{R + h_{ie}}$$

$$D = 1 + R_M \beta$$

$$R_{Mf} = \frac{R_M}{D} = \frac{V_o}{I_S}$$

$$A_{Vf} = \frac{V_o}{V_S} = \frac{V_o}{I_S R_S} = A_{Vf} = \frac{R_{Mf}}{R_S}$$

$$R_{if} = \frac{R_i}{D} \quad R_i = \frac{R_{if} h_{ie}}{R + h_{ie}}$$


$$R_{of} = \frac{R_o}{1 + R_{mp}\beta}$$

R_o : open R_C

$$R_o = R'$$

$$R_m = \frac{R_f}{R_L \rightarrow \infty} \quad R_N$$

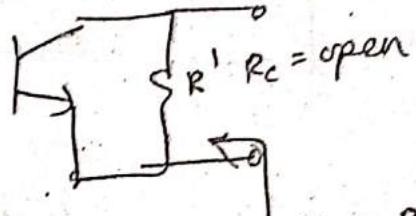when $R_C \rightarrow \infty \quad R_L = R'$




$$\therefore R_{mp} = -\frac{h_{fe} R' R}{R + h_{ie}} \quad \text{when } R_C \rightarrow \infty \quad R_L = R'$$

$$R_{of} = \frac{R_o}{1 + R_{mp}\beta}$$

$$R_{of} = R_{of} || R_C$$

(4)

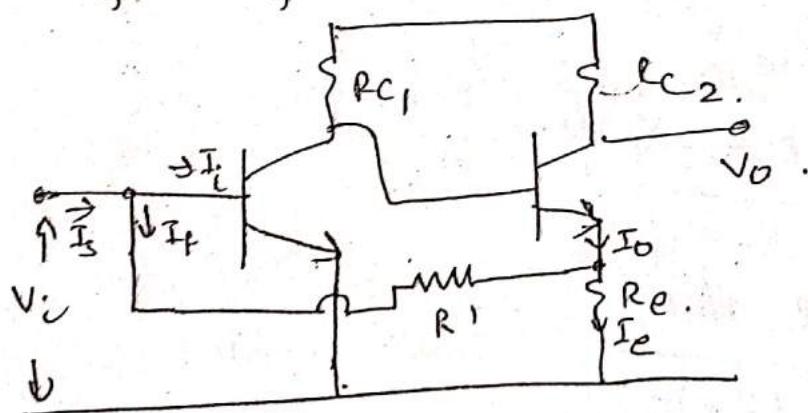

$$\begin{aligned} &I_o \downarrow I_f \\ &\text{---} \\ &I_{eb} \downarrow \\ &I_o + I_f = I_e \\ &I_f = I_b + I_e \\ &-I_f + I_o \end{aligned}$$

- ④ Identifying the topology:
- i) as feedback resistor R_f is directly connected to the base shunt mixing
 - or as feedback signal is I_f ∵ shunt mixing

$$I_f = \frac{(V_{L1} - V_e)}{R'}$$

$$I_f = -\frac{V_e}{R'}$$

$$\approx \frac{(I_0 - I_f) R_e}{R'}$$

$$I_f (R_e + R') = I_0 R_e$$

$$I_f = \frac{R_e}{R_e + R'} I_0$$

$$\Rightarrow I_f \propto I_0$$

current sampling


current shunt feedback amplifier

② for draw o/p drop

$$\text{set } I_0 = 0$$

o/p drop

$$\text{set } V_{L1} = 0$$

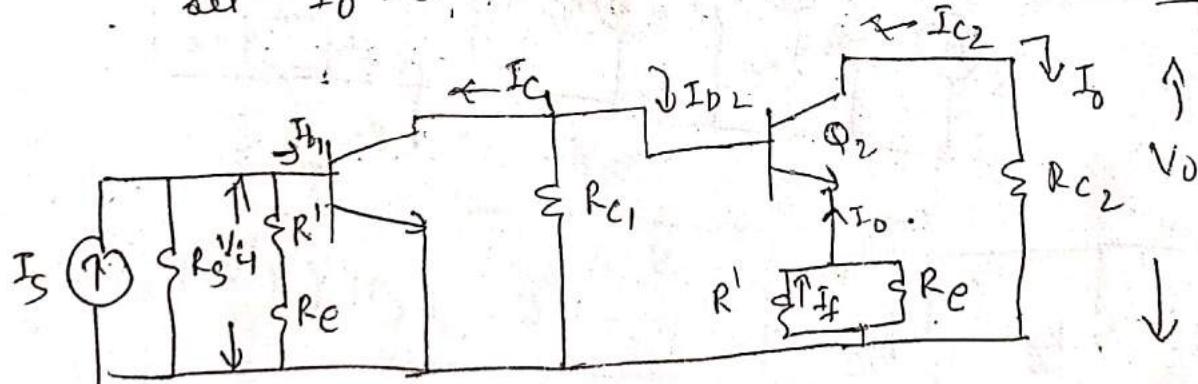

$$I_f = I_0 \times \frac{R_e}{R' + R_e}$$

$$\frac{I_f}{I_0} = \frac{R_e}{R' + R_e}$$

$$\Rightarrow \beta = \frac{R_e}{R' + R_e}$$

$$A_I = \frac{I_0}{I_S} = -\frac{I_{C2}}{I_S}$$

$$= -\frac{I_{C2}}{I_{B2}} \times \frac{I_{B2}}{I_{C1}} \times \frac{I_{C1}}{I_{B1}} \times \frac{I_{B1}}{I_S}$$


Suresh
Engineer.

2500

$$\rightarrow \frac{-I_{C2}}{I_{B2}} = \frac{-h_{fe} I_{B2}}{I_{B2}} = -h_{fe}$$



$$\rightarrow \frac{I_{C1}}{I_{B1}} = \frac{h_{fe} I_{B1}}{I_{B1}} = h_{fe}$$
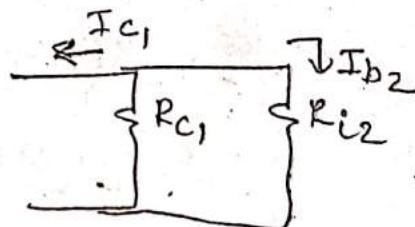
$$I_{B2} = -I_{C1} \times \frac{R_{C1}}{R_{C1} + R_{i2}}$$



$$\rightarrow \frac{I_{B2}}{I_{C1}} = \frac{-R_{C1}}{R_{C1} + R_{i2}}$$
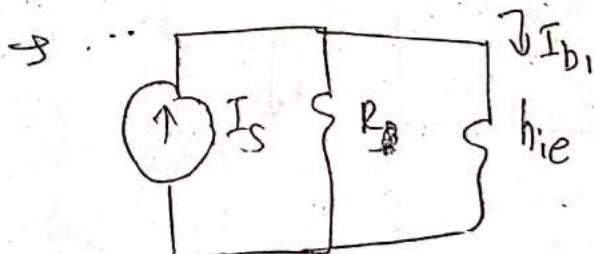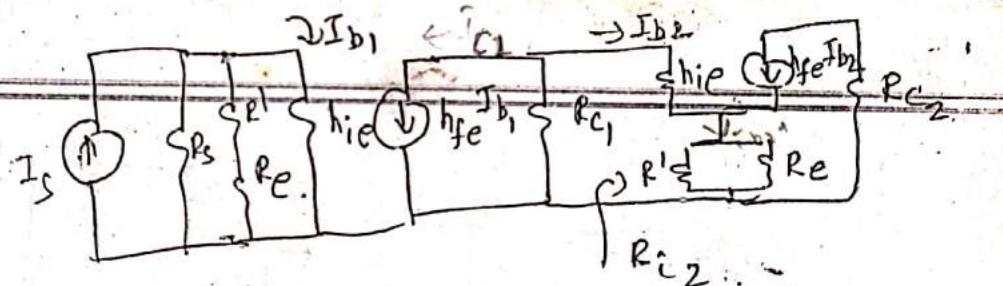
$$R_{i2} = h_{ie} + (1+h_{fe}) \frac{R'}{R_e}$$



$$R = R_s \parallel (R' + R_e)$$

$$V_{o2} = \frac{V_2}{I_2} = \frac{h_{ie} I_{B2} + (R' + R_e) V_2}{(h_{fe} + 1) I_2}$$

$$I_{B1} = I_S \times \frac{R}{R + h_{ie}} \Rightarrow \frac{I_{B1}}{I_S} \approx \frac{R}{R + h_{ie}}$$

$$\Rightarrow A_I = (-h_{fe})(h_{fe}) \left(\frac{-R_{C1}}{R_{C1} + R_{i2}} \right) \left(\frac{R}{R + h_{ie}} \right)$$

$$D = 1 + A_I \beta$$

$$A_{I_f} = \frac{A_I}{D}$$

$$A_{V_f} = \frac{V_o}{V_s} = -\frac{I_c R_{C_2}}{I_s R_S}$$

$$A_{V_f} = A_{I_f} \frac{R_{C_2}}{R_S}$$

$$\Rightarrow R_i = R_S \parallel (R^l + R_e) \text{ hie}$$

$$R_{i_f} = \frac{R_i}{D}$$


$$R_{o_f} = R_o (1 + A_I \beta) \Rightarrow R_o = \infty$$

$$R_{o_f}' = \frac{R_o' (1 + A_I \beta)}{1 + A_I \beta}$$

$$R_o' = R_{C_2}$$


$$\Rightarrow R_{o_f}' \approx R_{C_2}$$

$$g + V_{C_2}$$

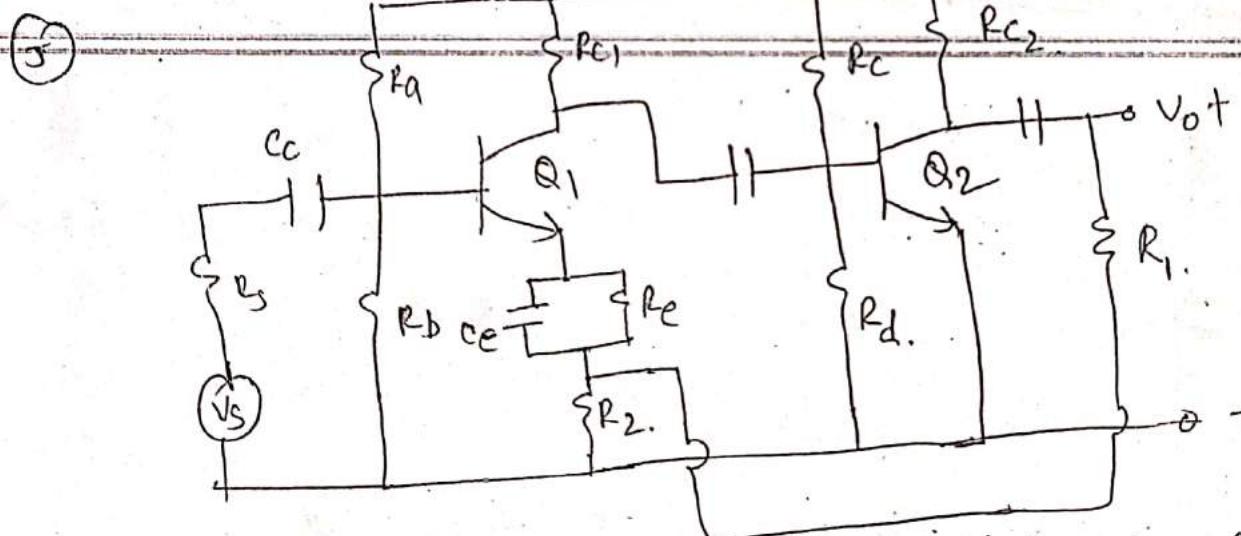


Voltage Series:

o/p loop $V_o = 0$

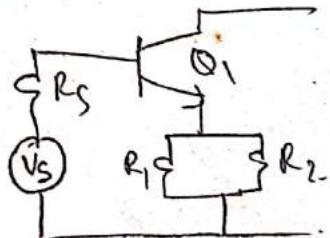

Neglecting R_a, R_b, R_c & R_d
cell R_e acts as
short chkd.


o/p loop $I_e = 0$

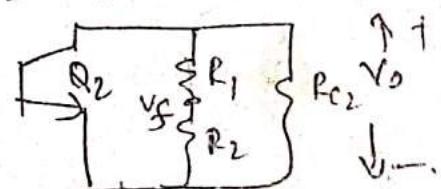

$$\beta = \frac{V_f}{V_o}$$

$$V_f = V_o \times \frac{R_2}{R_1 + R_2}$$
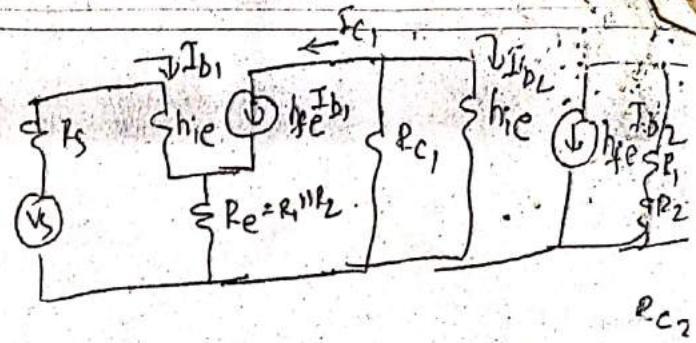
$$\Rightarrow \beta = \frac{V_f}{V_o} = \frac{R_2}{R_1 + R_2}$$



$$A_v = A_{v_1} \times A_{v_2}$$

$$A_{v_1} = A_{I_1} \times \frac{R_{L1}}{R_{i1}}$$

$$A_{v_1} = -h_{fe} \frac{R_{L1}}{R_{i1}}$$

where $R_{i1} = h_{ie} + (1+h_{fe})R_e$
where $R_e = R_1 || R_2$.

$$A_{v_2} = A_{I_2} \times \frac{R_{L2}}{R_{i2}}$$

$$R_{L2} = (R_1 + R_2) || R_{c2}$$

$$R_{i2} = h_{ie}$$

$$\Rightarrow A_{v_2} = -h_{fe} \times \frac{R_{L2}}{h_{ie}}$$

$$R_e = R_s + h_{ie} + (1+h_{fe})(R_1 || R_2)$$

$$R_{if} = R_i D$$

$$R_{of} = \frac{R_o}{1 + A_v \beta} \quad R_{c2} \text{ open}$$

$$\text{then } R_o = R_1 + R_2$$

$$R_{of}' = R_{of} || R_{c2}$$