

Tutorial - I Problems

- ① A CE transistor amplifier is driven by a voltage V_s of internal resistance $R_s = 800\Omega$. The load impedance is a resistor $R_L = 2000\Omega$. The parameters are $h_{ie} = 1100\Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$, $h_{oe} = 25 \times 10^{-6}$. Compute the current gain A_I , voltage gain A_V , overall current gain A_{IS} , overall voltage gain A_{VS} , input impedance R_i , output impedance Z_o , and the operating power gain A_p .

Sol: Current gain $A_I = \frac{-h_{fe}}{1 + h_{oe} R_L} = \frac{-50}{1 + (25 \times 10^{-6}) \times 2000} = -47.6$

Input impedance $R_i = h_{ie} + h_{re} A_I R_L = 1100 + (2.5 \times 10^{-4}) (-47.6) 2000 = 1076\Omega$

Voltage gain $A_V = \frac{A_I R_L}{R_i} = \frac{-47.6 \times 2000}{1076} = -88.47$

Overall voltage gain $A_{VS} = \frac{A_V R_i}{R_i + R_s} = \frac{(-88.47) \times 1076}{1076 + 800} = -50.75$

Overall Current gain $A_{IS} = \frac{A_I R_s}{R_i + R_s} = \frac{-47.6 \times 800}{1076 + 800} = -20.30$

output admittance $Y_o = h_{oe} - \frac{h_{fe} h_{re}}{h_{ie} + R_s}$
 $= (25 \times 10^{-6}) - \frac{50 \times 2.5 \times 10^{-4}}{(1100 + 800)} = 18.42 \times 10^{-6} S$

Hence

$$Z_o = \frac{1}{Y_o} = \frac{10^6}{18.42} = 0.0543 \times 10^6 \Omega = 54.31 k\Omega$$

Power gain

$$A_p = A_V \cdot A_I = 88.47 \times 47.6 = 4211$$

A transistor in CB Configuration is driven by a voltage source V_s of internal resistance $R_s = 800\Omega$. The load impedance is a resistor $R_L = 2000\Omega$. The h-Parameters are $h_{ib} = 22\Omega$, $h_{rb} = 3 \times 10^{-4}$, $h_{fb} = -0.98$ and $h_{ob} = 0.5 \mu A/V$. Compute the current gain A_I , input resistance R_i , voltage gain A_v , overall voltage gain A_{vs} , overall current gain A_{is} , output impedance Z_o & operating power gain A_p .

$$\text{Current gain } A_I = \frac{-h_{fb}}{1 + h_{ob} \cdot R_L} = \frac{-(-0.98)}{1 + (0.5 \times 10^{-6}) \times 2000} = 0.98$$

$$\text{Input impedance } R_i = h_{ib} + h_{rb} \cdot A_I \cdot R_L = 22 + 3 \times 10^{-4} \times 0.98 \times 2000 = 22.59\Omega$$

$$\text{Voltage gain } A_v = \frac{A_I \cdot R_L}{R_i} = \frac{0.98 \times 2000}{22.59} = 86.78$$

$$\text{Overall voltage gain } A_{vs} = \frac{A_v \cdot R_i}{R_i + R_s} = \frac{86.78 \times 22.59}{22.59 + 800} = 2.383$$

$$\text{Overall current gain } A_{is} = \frac{A_I \cdot R_s}{R_i + R_s} = \frac{0.98 \times 800}{22.59 + 800} = 0.953$$

$$\begin{aligned} \text{Output admittance } Y_o &= h_{ob} - \frac{h_{fb} \cdot h_{rb}}{h_{ib} + R_s} \\ &= (0.5 \times 10^{-6}) - \frac{(-0.98) \times 3 \times 10^{-4}}{22 + 800} = 0.8576 \times 10^{-6} S \end{aligned}$$

$$\text{Hence } Z_o = \frac{1}{Y_o} = \frac{10^6}{0.8576} \Omega = 1.166 \times 10^6 \Omega$$

$$\text{Power gain } A_p = A_v \cdot A_I = 86.78 \times 0.98 = 85.04$$

3) A CC transistor amplifier is driven by a voltage source of internal resistance $R_S = 800\Omega$. The load impedance is a resistor $R_L = 2000\Omega$. The h-Parameters are $h_{ic} = 1100\Omega$, $h_{rc} = \frac{1}{1100}$, $h_{fc} = -51$ & $h_{oc} = 25\mu A/V$. Compute A_I , R_i , A_V , A_{VS} , A_{IS} , Z_o , A_P .

$$\text{Current gain } A_I = \frac{-h_{fc}}{1 + h_{oc} R_L} = \frac{-(-51)}{1 + (25 \times 10^{-6} \times 2000)} = \frac{51}{1.05} = 48.57$$

$$\text{Input impedance } R_i = h_{ic} + h_{rc} \cdot A_I \cdot R_L = 1100 + \left(\frac{1}{1100} \times 48.57 \times 2000 \right) = 98,240\Omega$$

$$\text{Voltage gain } A_V = \frac{A_I \cdot R_L}{R_i} = \frac{48.57 \times 2000}{98,240} = 0.9888$$

$$\text{Overall voltage gain } A_{VS} = \frac{A_V \cdot R_i}{R_i + R_S} = \frac{0.988 \times 98,240}{98,240 + 800} = 0.981$$

$$\text{Overall current gain } A_{IS} = \frac{A_I \cdot R_S}{R_i + R_S} = \frac{48.57 \times 800}{98,240 + 800} = 0.3923$$

$$\begin{aligned} \text{output admittance } Y_o &= h_{oc} - \frac{h_{fc} \cdot h_{rc}}{h_{ic} + R_S} \\ &= (25 \times 10^{-6}) - \frac{(-51)(1)}{1100 + 800} = 26.86 \times 10^{-3} \end{aligned}$$

Hence output impedance

$$Z_o = \frac{1}{Y_o} = \frac{10^3}{26.86} \Omega = 37.28\Omega$$

Power gain

$$A_P = A_I \cdot A_V = 48.57 \times 0.9888 = 48.04$$

Approximate Conversion Formulas for Hybrid Parameters

The expression for CE Parameters in terms of the CB Parameters may be obtained from Table given below by interchanging the subscripts b & e

CE

CC

CB

h_{ie}

$$h_{ic} = h_{ie}$$

$$h_{ib} = \frac{h_{ie}}{1+h_{fe}}$$

h_{fe}

$$h_{fc} = -(1+h_{fe})$$

$$h_{fb} = -\frac{h_{fe}}{1+h_{fe}}$$

h_{re}

$$h_{rc} = 1$$

$$h_{rb} = \frac{h_{ie} h_{oe}}{1+h_{fe}} - h_{re}$$

h_{oe}

$$h_{oc} = h_{oe}$$

$$h_{ob} = \frac{h_{oe}}{1+h_{fe}}$$

Three derivati Formula
In exam CE, CB, CC Formula can be written as

$$\text{CE } A_I = \frac{-h_{fe}}{1+h_{oe}R_L}$$

$$Z_i = h_{ie} + h_{re} A_I Z_L$$

$$Y_o = h_{oe} - \frac{h_{re} h_{fe}}{h_{ie} + R_s} = \frac{1}{Z_o}$$

$$A_v = \frac{A_I Z_L}{Z_i}$$

$$A_{vs} = \frac{A_v Z_i}{Z_i + R_s}$$

$$A_{vs} = \frac{A_I R_s}{Z_i + R_s}$$

CB

$$A_I = \frac{-h_{fb}}{1+h_{ob}R_L}$$

CC

$$\frac{-h_{fc}}{1+h_{oc}R_L}$$