

Tutorial - Unit-3 Feedback Amplifier

- 1) A negative feedback amplifier in voltage-series configuration feeds 10% of the output back to the input. Voltage gain of the amplifier without feedback is 100. Input & output resistance are $10\text{K}\Omega$ & $1\text{K}\Omega$ resp.
Find i. Reduction in voltage gain, input resistance & o/p resistance with feedback

Sol:- Given openloop gain $A = 100$

feedback Ratio $\beta = 10\% = 0.1$

i/p impedance without feedback $Z_{in} = 10\text{K}\Omega$

o/p impedance without feedback $Z_{out} = 1\text{K}\Omega$

\Rightarrow closed loop voltage gain $A_f = \frac{A}{1+A\beta} = 9.09$

% reduction in voltage gain

$$= \frac{A - A_f}{A} \times 100 = 90.9\%$$

\Rightarrow Input impedance with feedback

$$Z_{inf} = (1+A\beta) Z_{in} = 110\text{K}\Omega$$

% ~~re~~ increment in input impedance

$$\Rightarrow \frac{Z_{inf} - Z_{in}}{Z_{in}} \times 100 = 1000\%$$

\Rightarrow output impedance with feedback

$$Z_{out-f} = \frac{Z_{out}}{1+A\beta} = \frac{1}{11}$$

% reduction in o/p impedance

$$\frac{Z_{out} - Z_{out-f}}{Z_{out}} \times 100 = 90.91\%$$

2) An amplifier has a mid freq gain of 1000 and a bandwidth of 500 kHz

(1) What will be the new bandwidth & gain, if 10% negative feedback is given.

(2) What should be the amount of feedback if the bandwidth is to be restricted to 1 MHz.

Sol:- given mid freq gain = $A = 1000$

B.W without feedback = 500 kHz

feedback ratio $\beta = 10\% = 0.1$

$$\Rightarrow (i) B.W_f = (1 + A\beta) B.W$$

gain with feedback

$$A_f = \frac{A}{1 + A\beta}$$

(ii) Feedback ratio to restrict the bandwidth to 1 MHz (2)

$$\beta = \frac{\frac{B.W_f}{B.W} - 1}{A} =$$

3) To amplifier of 60 dB gain a feedback $\beta = 0.006$ is applied. What would be the change in the overall gain of the feedback amplifier if the gain of the amplifiers decreases by 15%.

Sol:- $A = 60 \text{ dB} = 1000$ $\beta = 0.006$

$$A_{f1} = \frac{1000}{1 + A\beta} = 142.8$$

$$A_{f2} \Rightarrow \text{if } A \text{ is reduce } 15\% = 1000 - 150 = 850$$

$$A_{f2} = \frac{850}{1 + A\beta} = 139.34$$

$$\Rightarrow \text{Change of overall gain} \Rightarrow \frac{A_{f1} - A_{f2}}{A_{f1}} \times 100 = \underline{\underline{2.42\%}}$$